

## Study of Basic OPAMP Configurations and Simple Mathematical Operations


### Objectives:

- (I) Study of the inverting amplifier configuration and to find its gain
- (II) Study of the non-inverting amplifier configuration and to find its gain
- (III) Study simple mathematical operation and design an averaging amplifier


**Components:** OPAMP 741 chip, Resistors, Oscilloscope, DC voltage source, Bread board

**Theory:** Please refer the supplementary note.

### Circuit Diagram:

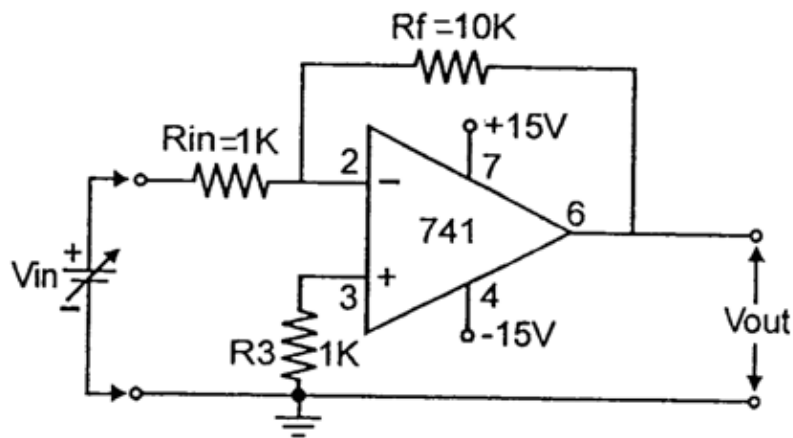

**Inverting amplifier**

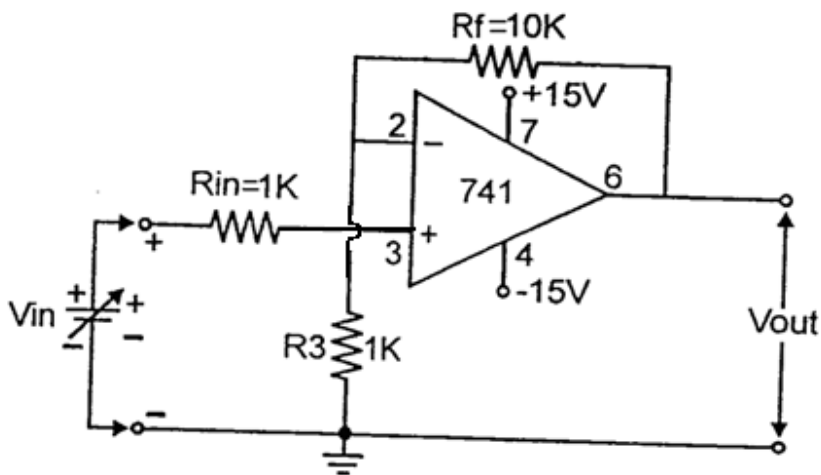

**Non-inverting amplifier**

### Procedure:

**(I) Inverting amplifier**

1. Configure the circuit as shown in the circuit diagram. Connect the pins 7 and 4 of the IC to the  $\pm 15\text{V}$  output terminals of the D.C. power supply. Connect the 0V terminal to ground. Choose  $R_{in} = 1\text{K}\Omega$  and  $R_f = 10\text{K}\Omega$ . Measure the resistance values with multimeter and calculate gain,  $-(R_f/R_{in})$ . Connect a resistor  $R_3 (= R_{in} \parallel R_f \approx R_{in})$  as shown in the circuit diagram so as to minimize offset due to input bias current.
2. Connect one of the output terminals of the D.C. power supply (0-30V) at the **inverting input (pin no. 2)**.
3. Switch on the power supply and apply different voltages in the range 0- 1.5V (why?) in steps of 0.2 V at the inverting terminal. Measure this input using a digital multimeter.
4. Measure the corresponding output voltages with the multimeter and calculate gain  $V_o/V_{in}$ . Note the sign of the output voltage.
5. Now, replace  $R_f$  by  $50\text{K}\Omega$ . Measure the resistance value with multimeter and calculate gain,  $-(R_f/R_{in})$ .
6. Apply different voltages in the range 0- 0.5V in steps of 0.1 V at the inverting terminal. Measure this input using a digital multimeter.
7. Measure the corresponding output voltages with the multimeter and calculate gain  $V_o/V_{in}$ .
8. Plot graphs for  $V_{in} \sim V_o$  for both the values of  $R_f$ .
9. You may also use a function generator to give a sinusoidal input and notice the output waveform using an oscilloscope.

**(II) Non-inverting amplifier**

1. Configure the circuit as shown in the circuit diagram with  $R_{in} = 1\text{K}\Omega$  and  $R_f = 10\text{K}\Omega$ . using the measured value of resistance calculate gain,  $1 + (R_f/R_{in})$ .
2. Connect one of the output terminals of the D.C. power supply (0-30V) at the **non-inverting input (pin no. 3)**.
3. Repeat steps 3 onwards of procedure (I) with inputs applied at non-inverting terminal.

**Observations**

**Table (I):**

Obs. No.	Input (V)	$-\frac{R_f}{R_{in}} = \text{-----}$			$-\frac{R_f}{R_{in}} = \text{-----}$		
		Output (V)	Gain $V_o/V_{in}$	Average	Output (V)	Gain $V_o/V_{in}$	Average
	0.2						
	0.4						
	...						


**Table (For II):**

Obs. No.	Input (V)	$1 + \frac{R_f}{R_{in}} = \text{-----}$			$1 + \frac{R_f}{R_{in}} = \text{-----}$		
		Output (V)	Gain $V_o/V_{in}$	Average	Output (V)	Gain $V_o/V_{in}$	Average
1	0.1						
2	0.2						
..	...						

### (III) Simple mathematical operations using OPAMP

#### a. To study OPAMP as summing amplifier

Circuit Diagram:

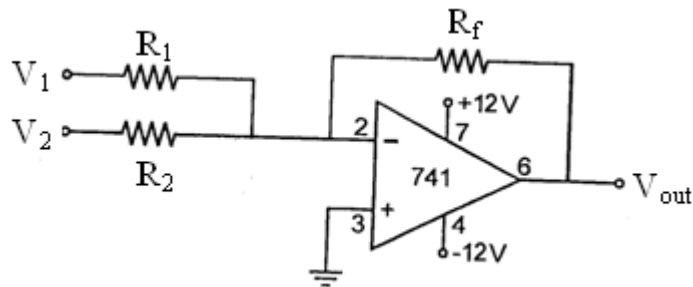

#### Procedure:


1. Assemble the circuit as shown in circuit diagram choosing  $R_1, R_2, R_f = 10K\Omega$  each. Use 0- $\pm 15V$  terminal output to provide supply to the IC.
2. Using 0 – 30V and 5V terminals of the power supply, apply two inputs at the inverting terminal. Measure each input with multimeter.
3. Measure the output with multimeter for at least five input combinations.
4. Compare the output with the sum of the two inputs.

#### Observations:

Obs.No	$V_1$ (V)	$V_2$ (V)	$V_{out}$ (V)	$V_1 + V_2$ (V)
1				
..				
5				

#### b. To study OPAMP as difference amplifier

**Circuit Diagram:**

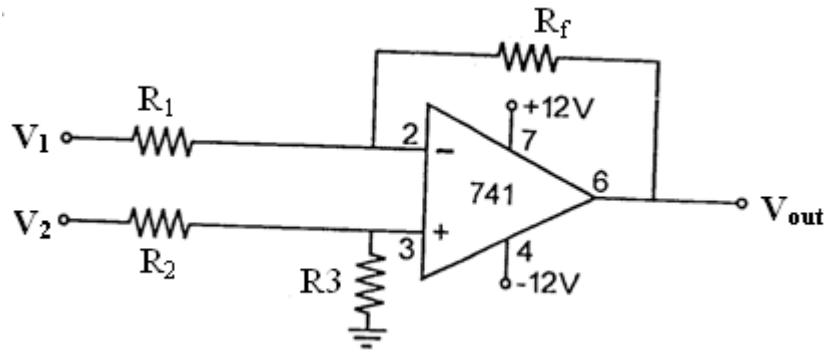

**Procedure:**

1. Assemble the circuit as shown in circuit diagram choosing  $R_1, R_2, R_3, R_f = 10K\Omega$  each. Use  $0- \pm 15V$  terminal output to provide supply to the IC.
2. Using  $0 - 30V$  and  $5V$  terminals of the power supply, apply two inputs, one at the inverting and the other at the non-inverting terminal. Measure each input with multimeter.
3. Measure output with multimeter for at least five input combinations.
4. Compare the output with the difference of the two inputs.

**Observations:**

Obs.No	$V_1$ (V)	$V_2$ (V)	$V_{out}$ (V)	$V_2 - V_1$ (V)
1				
..				
5				

- c. Inverting amplifier configuration of OPAMP is nothing but multiplication or division of input voltage with a number equal to  $R_f/R_1$ . With the knowledge of division and addition design an averaging amplifier of inputs  $V_1$  and  $V_2$  and tabulate.

**Conclusions:**

---